

CS 223 DIGITAL DESIGN
SECTION 5 LAB 2


ÖMER OKTAY GULTEKIN

21901413

18.10.2021

~~CS 223~~

* FULL-ADDER CIRCUIT SCHEMATICS :

 

IC LIST


- ① One IC-7408 QUAD 2-input AND Gate
- ② One IC-7432 QUAD 2-input OR Gate
- ③ One IC-7486 QUAD 2-input X-OR Gate

* 74HC86
GND-7
Vcc-14

* 74HC08
GND-7
Vcc-14

* 74HC32
GND-7
Vcc-14

* TWO-BIT ADDER CIRCUIT SCHEMATICS:

 

IC LIST

- ① One IC-7408 AND Gate
 - ② One IC-7432 OR Gate
 - ③ One IC-7486 X-OR Gate
- } Each have 4 corresponding gates

* 74HC86

GND (0V) - 7

V_{CC} (+5V) - 14

* 74HC08

GND (0V) - 7

V_{CC} (+5V) - 14

* 74HC32


GND (0V) - 7

V_{CC} (+5V) - 14

LAB CALCULATOR CIRCUIT SCHEMATICS

IC LIST

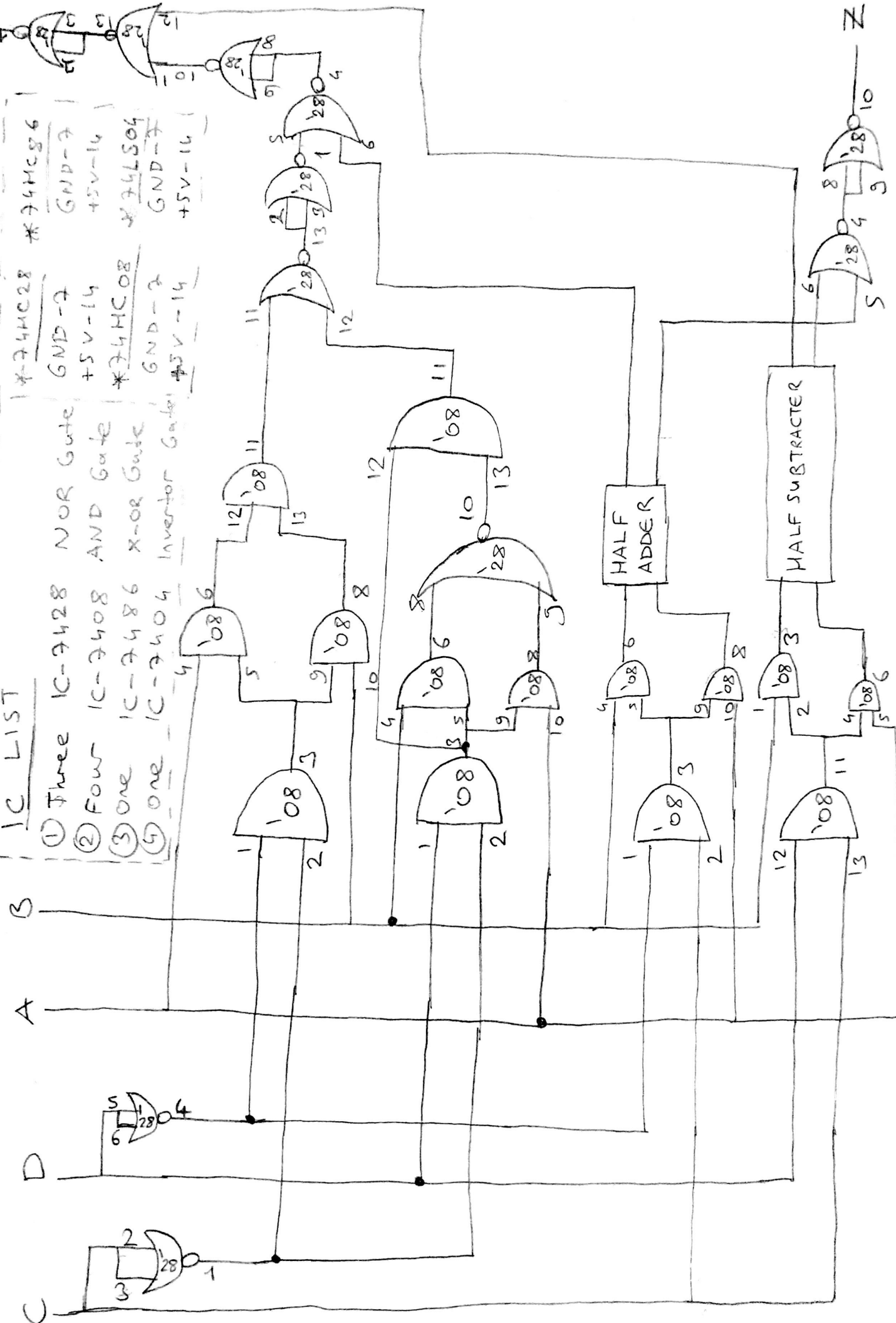- ① Three IC-7428 NOR Gate *74HC28 GND-7 +5V-14
- ② Four IC-7408 AND Gate *74HC08 GND-7 +5V-14
- ③ One IC-7486 X-OR Gate *74LS04 GND-7 +5V-14
- ④ One IC-7404 Inverter Gate *74HC08 GND-7 +5V-14



* Behavioral system Verilog for the full adder and a testbench for it

timescale 1ns/1ps

module fulladder(

input logic a, b, cin,

output logic s, cout

);

logic p, g;

assign p = a ^ b;

assign g = a & b;

assign s = p ^ cin;

assign cout = g | (p & cin);

endmodule

• Test Bench:

timescale 1ns/1ps

module testbench1();

logic a, b, cin;

logic s, cout;

fulladder adder(a, b, cin, s, cout);

initial begin

a = 0; b = 0; cin = 0; #10;

if (s != 0 & cout != 0) \$display("000 failed");

cin = 1; #10;

if (s != 1 & cout != 0) \$display("001 failed"); ^{→ I will omit if 's}

b = 1; #10;

cin = 0; #10;

a = 1; #10;

b = 0; #10;

cin = 1; #10;

b = 1; #10;

end

endmodule

* Structural SystemVerilog Module For The Full Adder And Testbench for It

timescale 1ns/1ps
module structuralfulladder(

input logic a, b, cin,

output logic s, cout;
);

logic n1, n2, n3;

halfadder ha1(a, b, n1, n2);

halfadder ha2(n1, cin, s, n3);

Or2 or1(n2, n3, cout);

endmodule

module halfadder(input logic a, b, output logic sum, cout);

and2 and1(a, b, cout);

xor2 xor1(a, b, sum);

endmodule

module and2(input logic a, b, output logic c);

assign c = a & b;

endmodule

module xor2(input logic a, b, output logic c);

assign c = a ^ b;

endmodule

module Or2(input logic a, b, output logic c);

assign c = a | b;

endmodule

* Testbench

module testbench();

logic a, b, cin;

logic s, cout;

structuralfulladder adder(a, b, cin, s, cout);

initial begin

a=0; b=0; cin=0; #10;

cin=1; #10;

b=1; #10;

cin=0; #10;

a=1; #10;

b=0; #10;

cin=1; #10;

b=1; #10;

endmodule

* Structural systemverilog module for the 2-bit adder and testbench for it using the full adder module

'timescale 1ns / 1ps

module adder2bit(

input logic a0, a1, b0, b1, cin,
output logic s0, s1, cout
);

logic n1;

structural fulladder fulladder1(a0, b0, cin, s0, n1);

structural fulladder fulladder2(a1, b1, n1, s1, cout);

endmodule

• Testbench

'timescale 1ns / 1ps

module testbench3();

logic a0, b0, a1, b1, cin;

logic s0, s1, cout;

adder2bit adder(a0, a1, b0, b1, cin, s0, s1, cout);

initial begin

a0 = 0; a1 = 0; b0 = 0; b1 = 0; cin = 0; #10;

f { cin = 1; #10

b1 = 1; #10

cin = 0; #10

b0 = 1; #10

cin = 1; #10

b1 = 0; #10

cin = 0; #10

a1 = 1; b0 = 0; #10;

f → same as the above code block

a0 = 1; b0 = 0; #10

f

a1 = 0; b0 = 0; #10

f

end

endmodule

*Structural Systemverilog Module For The Lab Calculator And a Test Bench for it

```
'timescale 1ns / 1ps

module labcalculator(
    input logic a, b, c, d,
    output logic y, z);
    logic n1, n2, n3, n4, n5, n6, n7, n8, n9, n10, n11, n12, n13, n14,
    n15, n16, n17, n18, n19, n20, n21, n22, n23, n24, n25, n26, n27;

    nor2 NOR1(c, c, n1);
    nor2 NOR2(d, d, n2);
    and2 AND1(n1, n2, n3);
    and2 AND2(n3, a, n4);
    and2 AND3(n3, b, n5);
    and2 AND4(n4, n5, n6);
    and2 AND5(n1, d, n7);
    and2 AND6(n7, a, n8);
    and2 AND7(n7, b, n9);
    nor2 NOR3(n8, n9, n10);
    and2 AND8(n7, n10, n11);
    nor2 NOR4(n6, n11, n12);
    nor2 NOR5(n12, n12, n18);
    and2 AND9(n2, c, n13);
    and2 AND10(n13, a, n14);
    and2 AND11(n13, b, n15);
    halfadder adder(n14, n15, n16, n17);
    nor2 NOR6(n16, n18, n19);
    nor2 NOR7(n19, n19, n20);
    and2 AND12(c, d, n21);
    and2 AND13(n21, a, n22);
    and2 AND14(n21, b, n23);
    halfsubt subt(n22, n23, n24, n25);
    nor2 NOR8(n20, n24, n26);
    nor2 NOR9(n26, n26, y);
    nor2 NOR10(n17, n25, n27);
endmodule

module nor2(input logic a, b, output logic c);
    assign c = ~(a & b);
endmodule

module halfsubt(input logic a, b, output logic d, bout);
    assign d = a ^ b;
    assign bout = ~a & b;
endmodule
```


• TESTBENCH

'timescale 1ns / 1ps

module testbench4();

logic a, b, c, d;

logic y, z;

lab_calculator calculator(a, b, c, d, y, z);

initial begin

a = 0; b = 0; c = 0; d = 0; ~~a~~ 10;

d = 1; ~~a~~ 10;

c = 1; ~~a~~ 10;

d = 0; ~~a~~ 10;

b = 1; c = 0; ~~a~~ 10;

d = 1; ~~a~~ 1;

c = 1; ~~a~~ 1;

d = 0; ~~a~~ 1;

a = 1; c = 0; ~~a~~ 10;

d = 1; ~~a~~ 10;

c = 1; ~~a~~ 10;

d = 0; ~~a~~ 10;

b = 0; c = 0; ~~a~~ 10;

d = 1; ~~a~~ 10;

c = 1; ~~a~~ 10;

d = 0; ~~a~~ 10;

end

endmodule