

CS 223 Digital Design
Section 5 Lab 3

Ömer Oktay Gültekin

21901413
01.11.2021

~~Ömer Oktay Gültekin~~

* Behavioral SystemVerilog Module for a 2-to-4 decoder and a testbench for it

```
timescale 1ns/1ps
module decoder_2to4(
    input logic [1:0] d,
    input logic e,
    output logic [3:0] y
);

    assign y[0] = ~d[0] & ~d[1] & e;
    assign y[1] = d[0] & ~d[1] & e;
    assign y[2] = ~d[0] & d[1] & e;
    assign y[3] = d[0] & d[1] & e;

endmodule
```

• Testbench:

```
module decoder_test_bench();
    logic [1:0] d;
    logic e;
    logic [3:0] y;
    decoder_2to4 dec2(d, e, y);
    initial begin
        d = 0; e = 1; #10;
        d[0] = 1; #10;
        d[1] = 1; d[0] = 0; #10;
        d[0] = 1; #10;
        e = 0; #10;
        d[1] = 0; #10;
        d[0] = 0; #10;
        d[1] = 1; #10;
        d[1] = 1; #10;
    end
endmodule
```

* Behavioral SystemVerilog module for a 2-to-1 multiplexer

timescale 1ns/1ps

```
module mux2to1(input logic [1:0] d,  
               input logic s,  
               output logic z y);  
    assign y = s ? d[1] : d[0];  
endmodule
```

* Structural system Verilog Module for a 4-to-1 multiplexer by using three 2-to-1 multiplexers, and Testbench for it.

timescale 1ns/1ps


```
module mux4to1(input logic [3:0] d,  
               input logic [1:0] s,  
               output logic y):  
    logic [1:0] middle;  
    mux2to1 lowmux2(d[1:0], s[0], middle[0]);  
    mux2to1 highmux2(d[3:2], s[0], middle[1]);  
    mux2to1 finalmux2(middle[1:0], s[1], y);  
endmodule
```

• Testbench

timescale 1ns/1ps

```
module mux4to1-test-bench();  
    logic [3:0] d;  
    logic [1:0] s;  
    logic y;  
    mux4to1 mux4(d, s, y);  
    initial begin  
        s = 0; d = 1; #10;  
        d[0] = 0; #10;  
        s[0] = 1; d[0] = 1; #10;  
        d[1] = 0; #10;  
        s[1] = 1; s[0] = 0; d[1] = 1; #10;  
        d[2] = 0; #10;  
        s[0] = 1; d[2] = 1; #10;  
        d[3] = 0; #10;  
    end  
endmodule
```

 * Block diagram and structural System Verilog module of 8-to-1 MUX by using two 4-to-1 Mux modules, two AND gates, an Inverter, and an OR gate.



• System Verilog Module

```

module mux8to1(
    input logic [7:0] d,
    input logic [2:0] s,
    output logic y);
    logic low, high, n1, n2, s2b;
    mux4to1 lowmux4(d[3:0], s[1:0], low);
    mux4to1 highmux4(d[7:4], s[1:0], high);
    inv inv1(s[2], s2b);
    and2 andfirst(low, s2b, n1);
    and2 andsecondandsecond(high, s[2], n2);
    or2 or1(n1, n2, y);
endmodule

```

```

module and2(input logic a, b, output logic c);
    assign c = a & b;
endmodule

```

```

module or2(input logic a, b, output logic c);
    assign c = a | b;
endmodule


```

```

module inv(input logic a, output logic b);
    assign b = ~a;
endmodule

```

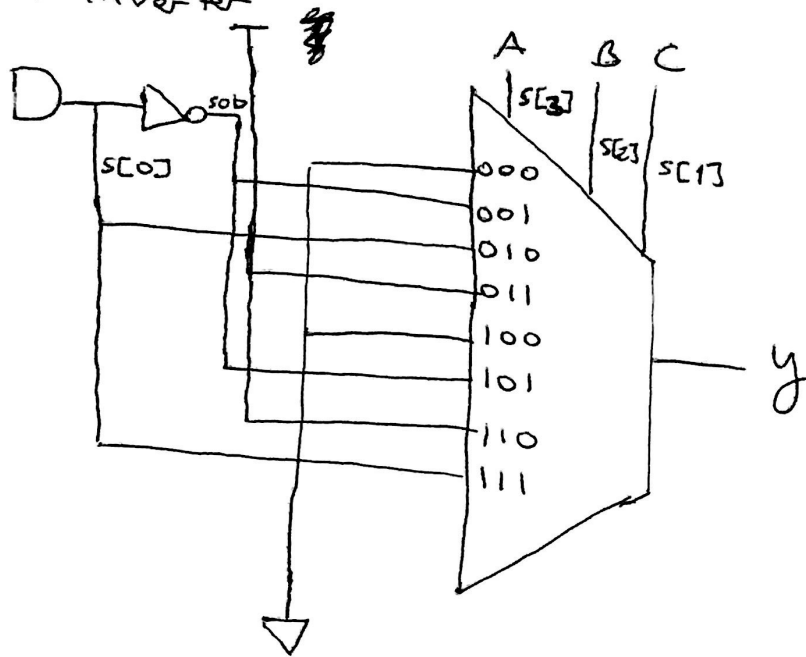* Block diagram and SystemVerilog module for $F(A, B, C, D) = \Sigma(2, 5, 6, 7, 10, 12, 13, 15)$ function using one 8-to-1 multiplexer and an inverter.



• SystemVerilog Module

```

module custom-module(
    input logic [3:0] s,
    output logic y);
    logic [7:0] d;
    logic sob;
    inv inv1(s[0], sob);
    assign d[0] = 0;
    assign d[1] = sob;
    assign d[2] = s[0];
    assign d[3] = 1;
    assign d[4] = 0;
    assign d[5] = sob;
    assign d[6] = 1;
    assign d[7] = s[0];
    mux8to1 mux8(d, s[3:1], y);
endmodule

```

```

module inv(input logic a, output logic b);
    assign b = ~a;
endmodule

```